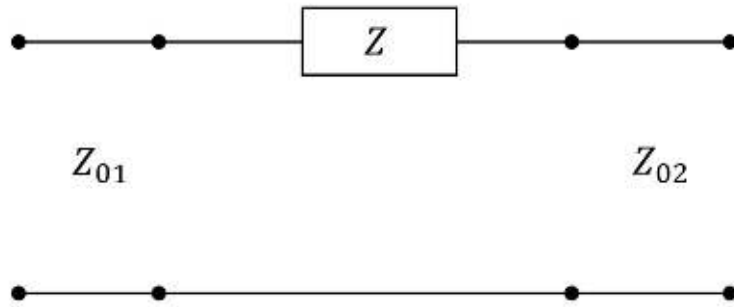


## 2 Homework Problems



## Homework Problem 1

1. Find the scattering parameter matrix of the following network.  
Assume  $Z_{01} = 50\Omega$ ,  $Z_{02} = 25\Omega$ ,  $Z = 10\Omega$




$$S_{11} = \left. \frac{V_1^-}{V_1^+} \right|_{z=0} \quad S_{21} = \left. \frac{V_2^-}{V_1^+} \right|_{z=0}$$

$$S_{12} = \left. \frac{V_1^-}{V_2^+} \right|_{z=0} \quad S_{22} = \left. \frac{V_2^-}{V_2^+} \right|_{z=0}$$

## Homework Problem 2

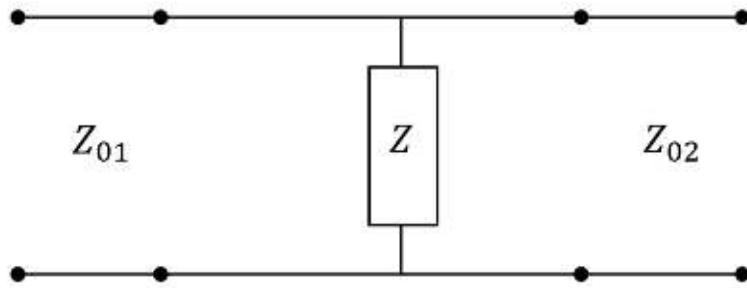2. Find the scattering parameter matrix of the following network.  
Assume  $Z_{01} = 50\Omega$ ,  $Z_{02} = 25\Omega$ ,  $Z = 10\Omega$




$$S_{11} = \left. \frac{V_1^-}{V_1^+} \right|_{z=0} \quad S_{21} = \left. \frac{V_2^-}{V_1^+} \right|_{z=0}$$

$$S_{12} = \left. \frac{V_1^-}{V_2^+} \right|_{z=0} \quad S_{22} = \left. \frac{V_2^-}{V_2^+} \right|_{z=0}$$

## Homework Problem 3

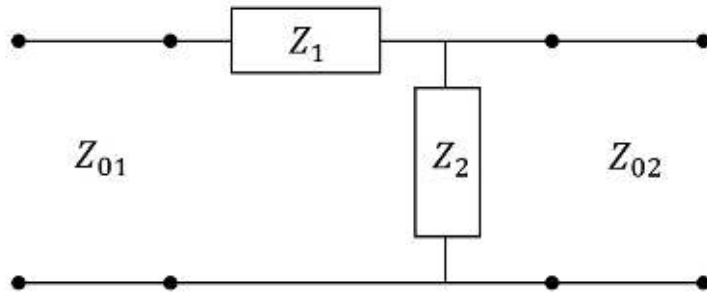3. Find the scattering parameter matrix of the following network.  
Assume  $Z_{01} = 50\Omega$ ,  $Z_{02} = 25\Omega$ ,  $Z_1 = 80\Omega$ ,  $Z_2 = 120\Omega$




$$S_{11} = \left. \frac{V_1^-}{V_1^+} \right|_{z=0} \quad S_{21} = \left. \frac{V_2^-}{V_1^+} \right|_{z=0}$$

$$S_{12} = \left. \frac{V_1^-}{V_2^+} \right|_{z=0} \quad S_{22} = \left. \frac{V_2^-}{V_2^+} \right|_{z=0}$$

## Homework Problem 4

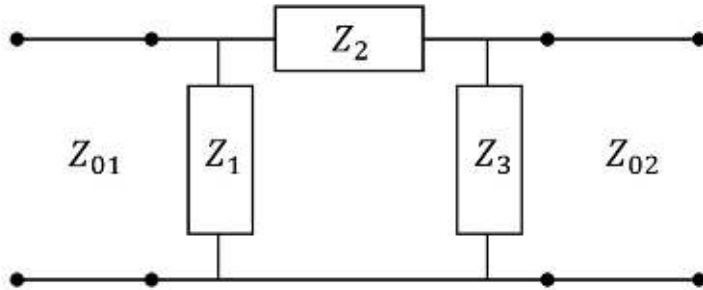4. Find the scattering parameter matrix of the following network.  
Assume  $Z_{01} = 50\Omega$ ,  $Z_{02} = 25\Omega$ ,  $Z_1 = 25\Omega$ ,  $Z_2 = 10\Omega$ ,  $Z_3 = 40\Omega$



$$S_{11} = \left. \frac{V_1^-}{V_1^+} \right|_{z=0} \quad S_{21} = \left. \frac{V_2^-}{V_1^+} \right|_{z=0}$$

$$S_{12} = \left. \frac{V_1^-}{V_2^+} \right|_{z=0} \quad S_{22} = \left. \frac{V_2^-}{V_2^+} \right|_{z=0}$$