

# Basics of S-parameters

## *Calculating The S-parameters*

Developed by Kathryn L. Smith, PhD





# Sources

*The material presented herein is from the following sources:*

***“Engineering Electromagnetics,” by Nathan Ida, 3<sup>rd</sup> ed. (2015)***

***“Antenna Theory,” by Constantine A. Balanis, 4<sup>th</sup> ed. (2016)***


***HFSS 2019 Help Files***

***“Elements of Electromagnetics,” by Matthew N.O Sadiku, 5<sup>th</sup> ed. (2010)***

***“Microwave Engineering,” by David Pozar, 4<sup>th</sup> ed. (2012)***


# / Calculating the S-Parameters (An Example)

Consider the following 2-port network:

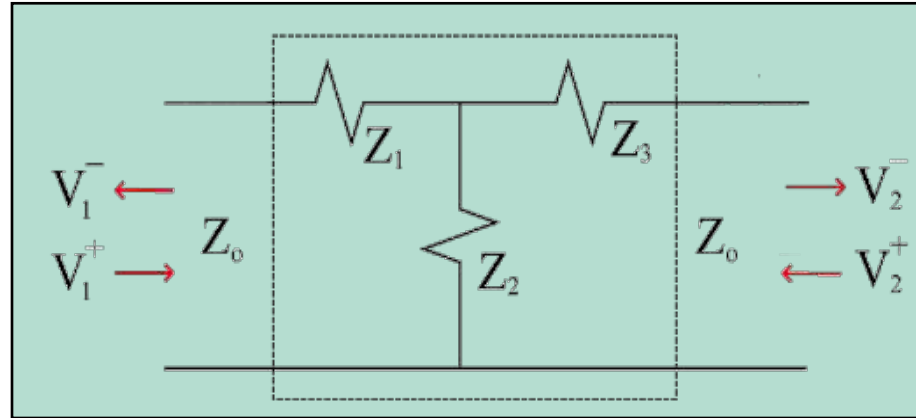


We will calculate the S-parameters of this network through a series of two measurements. For the first measurement, we will apply a test voltage at the first port, and match-terminate the second port. For the second measurement, we will apply a test voltage at the second port, and match terminate the first port.

**Measurement 1:**

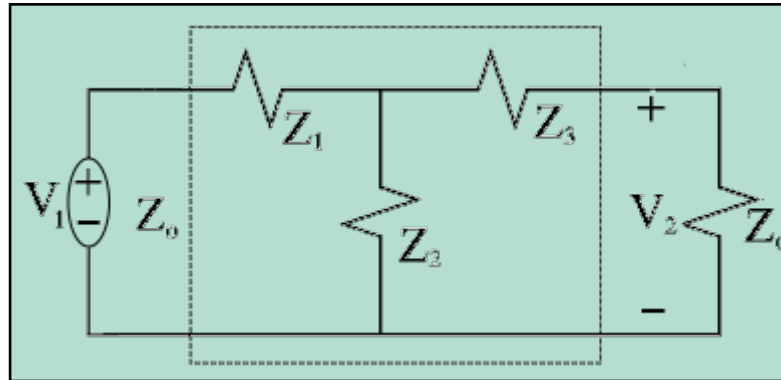


**Measurement 2**

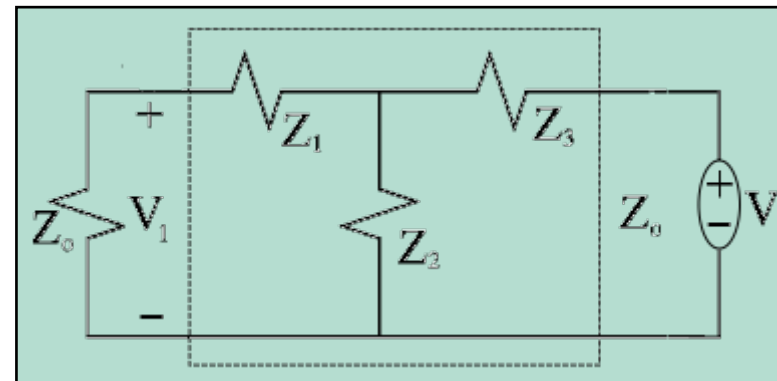

# Calculating the S-Parameters (An Example)

## Measurement 1:

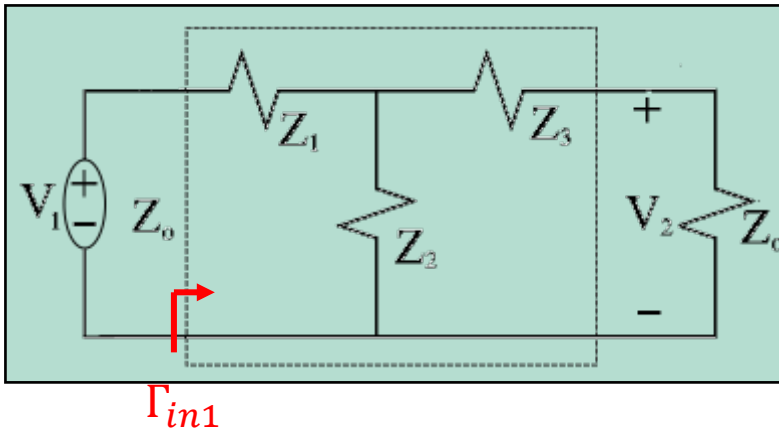

In order to calculate  $S_{11}$ , we can use the equation  $V_1^- = \Gamma_{in1} V_1^+$  together with the definition  $S_{11} = \frac{V_1^-}{V_1^+}$  (valid when port 2 is match-terminated) to show that, for this circuit configuration,  $S_{11} = \Gamma_{in1}$

We know that  $\Gamma_{in1} = \frac{Z_{in1} - Z_o}{Z_{in1} + Z_o}$ , and in this case,

$$Z_{in1} = Z_1 + (Z_o + Z_3) || Z_2 = Z_1 + \frac{Z_2 Z_3 + Z_2 Z_o}{Z_2 + Z_3 + Z_o}$$

So,


$$\Gamma_{in1} = \frac{Z_1 + (Z_o + Z_3) || Z_2 - Z_o}{Z_1 + (Z_o + Z_3) || Z_2 + Z_o}$$

And finally,

$$S_{11} = \frac{Z_1 + (Z_o + Z_3) || Z_2 - Z_o}{Z_1 + (Z_o + Z_3) || Z_2 + Z_o}$$

# Calculating the S-Parameters (An Example)

## Measurement 1:

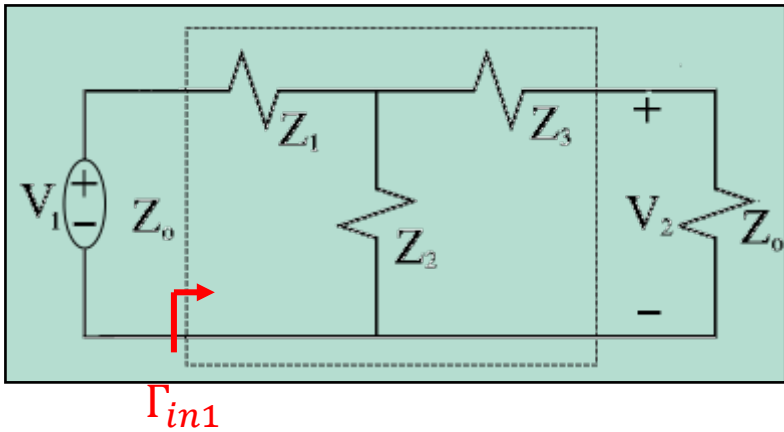

In order to calculate  $S_{21}$ , we use circuit analysis to show that:

$$V_2 = V_1 \left( \frac{Z_2 \parallel (Z_3 + Z_o)}{Z_1 + Z_2 \parallel (Z_3 + Z_o)} \right) \left( \frac{Z_o}{Z_3 + Z_o} \right)$$

And since, for this circuit configuration,

$$V_1 = V_1^+ (1 + S_{11}) \text{ and } V_2 = V_2^-$$

this becomes:


$$V_2^- = V_1^+ (1 + S_{11}) \left( \frac{Z_2 \parallel (Z_3 + Z_o)}{Z_1 + Z_2 \parallel (Z_3 + Z_o)} \right) \left( \frac{Z_o}{Z_3 + Z_o} \right)$$

so that,

$$S_{21} = \frac{V_2^-}{V_1^+} = (1 + S_{11}) \left( \frac{Z_2 \parallel (Z_3 + Z_o)}{Z_1 + Z_2 \parallel (Z_3 + Z_o)} \right) \left( \frac{Z_o}{Z_3 + Z_o} \right)$$

# Calculating the S-Parameters (An Example)

## Measurement 2

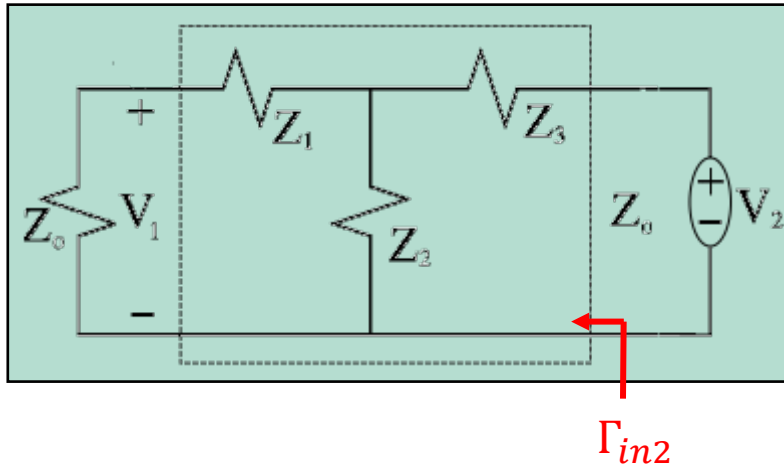

We can similarly calculate  $S_{22}$  using the equation  $V_2^- = \Gamma_{in2} V_2^+$  together with the definition  $S_{22} = \frac{V_2^-}{V_2^+}$  (valid when port 1 is match-terminated) to show that, for this circuit configuration,  $S_{22} = \Gamma_{in2}$

We know that  $\Gamma_{in2} = \frac{Z_{in2} - Z_o}{Z_{in2} + Z_o}$ , and in this case,

$$Z_{in2} = Z_3 + (Z_o + Z_1) || Z_2 = Z_3 + \frac{Z_2 Z_1 + Z_2 Z_o}{Z_2 + Z_1 + Z_o}$$

So,


$$\Gamma_{in2} = \frac{Z_3 + (Z_o + Z_1) || Z_2 - Z_o}{Z_3 + (Z_o + Z_1) || Z_2 + Z_o}$$

And finally,

$$S_{22} = \frac{Z_3 + (Z_o + Z_1) || Z_2 - Z_o}{Z_3 + (Z_o + Z_1) || Z_2 + Z_o}$$

# Calculating the S-matrix (An Example)

## Measurement 2

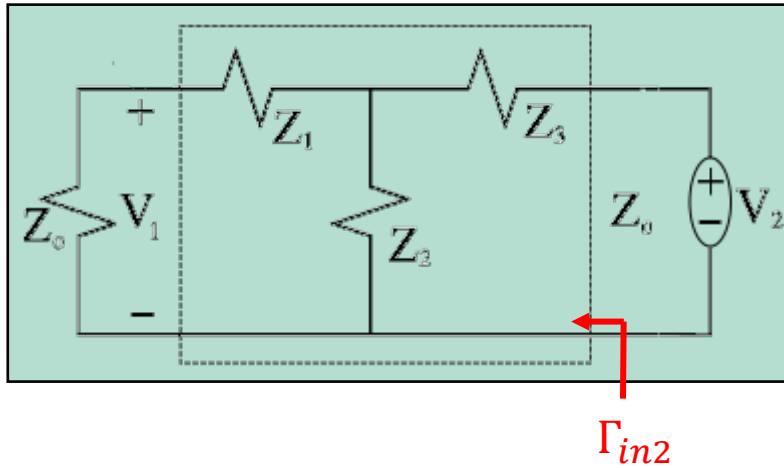

Finally, to calculate  $S_{12}$ , we use circuit analysis to show that:

$$V_1 = V_2 \left( \frac{Z_2 || (Z_1 + Z_o)}{Z_3 + Z_2 || (Z_1 + Z_o)} \right) \left( \frac{Z_o}{Z_1 + Z_o} \right)$$

And since, for this circuit configuration,

$$V_2 = V_2^+ (1 + S_{22}) \text{ and } V_1 = V_1^-$$


this becomes:

$$V_1^- = V_2^+ (1 + S_{22}) \left( \frac{Z_2 || (Z_1 + Z_o)}{Z_3 + Z_2 || (Z_1 + Z_o)} \right) \left( \frac{Z_o}{Z_1 + Z_o} \right)$$

so that,

$$S_{12} = \frac{V_1^-}{V_2^+} = (1 + S_{22}) \left( \frac{Z_2 || (Z_1 + Z_o)}{Z_3 + Z_2 || (Z_1 + Z_o)} \right) \left( \frac{Z_o}{Z_1 + Z_o} \right)$$
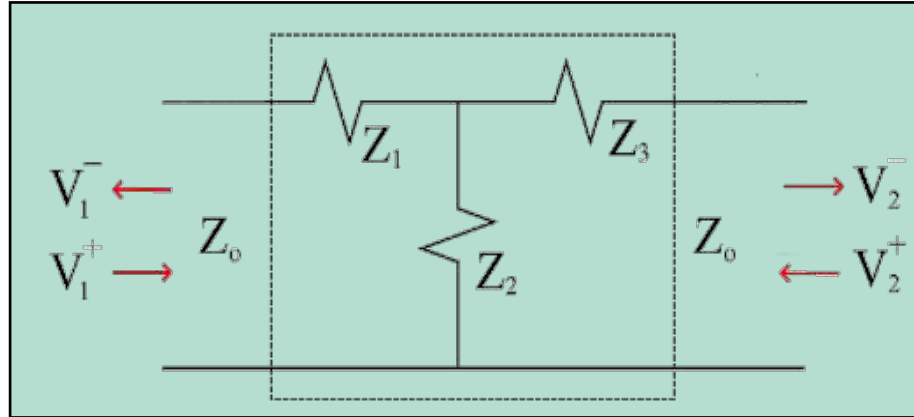
# Calculating the S-Parameters (An Example)



So the S-matrix for the above network is:

$$[S] = \begin{bmatrix} \frac{Z_1 + (Z_o + Z_3) \parallel Z_2 - Z_o}{Z_1 + (Z_o + Z_3) \parallel Z_2 + Z_o} & (1 + S_{22}) \left( \frac{Z_2 \parallel (Z_1 + Z_o)}{Z_3 + Z_2 \parallel (Z_1 + Z_o)} \right) \left( \frac{Z_o}{Z_1 + Z_o} \right) \\ (1 + S_{11}) \left( \frac{Z_2 \parallel (Z_3 + Z_o)}{Z_1 + Z_2 \parallel (Z_3 + Z_o)} \right) \left( \frac{Z_o}{Z_3 + Z_o} \right) & \frac{Z_3 + (Z_o + Z_1) \parallel Z_2 - Z_o}{Z_3 + (Z_o + Z_1) \parallel Z_2 + Z_o} \end{bmatrix}$$



 **Ansys**

